



Sheet (3) Electrical Transformers

- 11) The no-load current of a transformer is 10 A at a power factor of 0.25 lagging, when connected to 400 V, 50 Hz supply. Calculate:
- Magnetizing component of no-load current.
 - Iron loss and c) Maximum value of flux in the core assume that primary winding turns are 500.
- 12) A 15 kVA, 2200/110 V transformer has $R_1=1.75 \Omega$, $R_2=0.0045 \Omega$. The leakage reactances are $X_1=2.6 \Omega$ and $X_2=0.0075 \Omega$. Calculate:
- Equivalent resistance referred to primary
 - Equivalent resistance referred to secondary
 - Equivalent reactance referred to primary
 - Equivalent reactance referred to secondary
 - Equivalent impedance referred to primary
 - Equivalent impedance referred to secondary
 - Total copper loss
- 13) 250/125 V, 5 kVA single phase transformer has primary resistance of 0.2Ω and reactance of 0.75Ω . The secondary resistance is 0.05Ω and reactance of 0.2Ω .
- Determine its regulation while supplying full load on 0.8 leading p.f.
 - The secondary terminal voltage on full load and 0.8 leading p.f.
- 14) A 4 kVA, 200/400 V, 50 Hz, single phase transformer has equivalent resistance referred to primary as 0.15Ω . Calculate:
- The total copper loss on full load
 - The efficiency while supplying full load at 0.9 p.f lagging
 - The efficiency while supplying half load at 0.8 p.f lagging
- Assume total iron losses = 60 W.
- 15) A 5 kVA, 500/250 V, 50 Hz, single phase transformer gave the following readings,
- O.C. Test: 500 V, 1 A, 50 W (L.V. side open) $\rightarrow X_m, R_c$
S.C. Test: 25 V, 10 A, 60 W (L.V. side shorted) $\rightarrow R_g, X_g$
- Determine:
- η % on full load, 0.8 lagging p.f.
 - The voltage regulation on full load, 0.8 leading p.f.
 - η % on 60% of full load, 0.8 leading p.f.
 - Draw the equivalent circuit referred to primary and insert all the values in it.

P.161
6) The O.C. and S.C. tests on a 10 kVA, 125/250 V, 50 Hz, single phase transformer gave the following results:

O.C. Test: 125 V, 0.6 A, 50 W (on L.V. side)

S.C. Test: 15 V, 30 A, 100 W (on H.V. side)

Calculate:

- a) Copper loss on full load
- b) Full load η % at 0.8 leading p.f.
- c) Half load η % at 0.8 leading p.f.
- d) Regulation at full load, 0.9 leading p.f.

P.171
7) A 2500/250 V, 50 Hz, 50 kVA, single phase transformer has a resistance of 0.8Ω and 0.012Ω and a reactance of 4Ω and 0.04Ω for H.V. and L.V. windings respectively. Transformer gives 96% maximum efficiency at 75% full load at unity p.f. The magnetizing component of no load current is 1.2 A on 2500 V side. Find out ammeter, voltmeter and wattmeter readings on O.C and S.C. test if supply is given to the 2500 V side in both cases.

Best wishes

Course committee:

Dr. Abd El-Wahab Hasan

Eng. Mohamed Gamal

Eng. Kotb Mohamed


2013/2014

Problem ①

$I_0 = 10 \text{ A}$ at P.f.₀ = 0.25 lag, $V_1 = 400 \text{ V}$, $f = 50 \text{ Hz}$

Calculate:

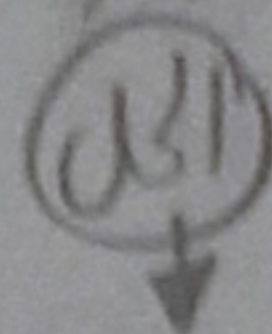- ① I_m ② Iron loss ③ Max. Value of flux in the core if $N_1 = 500$



① $I_m = I_0 \sin \phi_0 \quad \therefore \text{P.f.}_0 = \cos \phi_0$

$\phi_0 = \cos^{-1}(0.25) = 75.522^\circ$


$\therefore I_m = 10 \times \sin(75.522) = \boxed{9.6824 \text{ A}} \quad \# \text{ ①}$

② at no-load

$P_{\text{Iron}} = V_1 \times I_c$

$I_c = I_0 \cos \phi_0 = \boxed{2.5 \text{ A}}$

$P_{\text{Iron}} = 1000 \text{ Watt}$

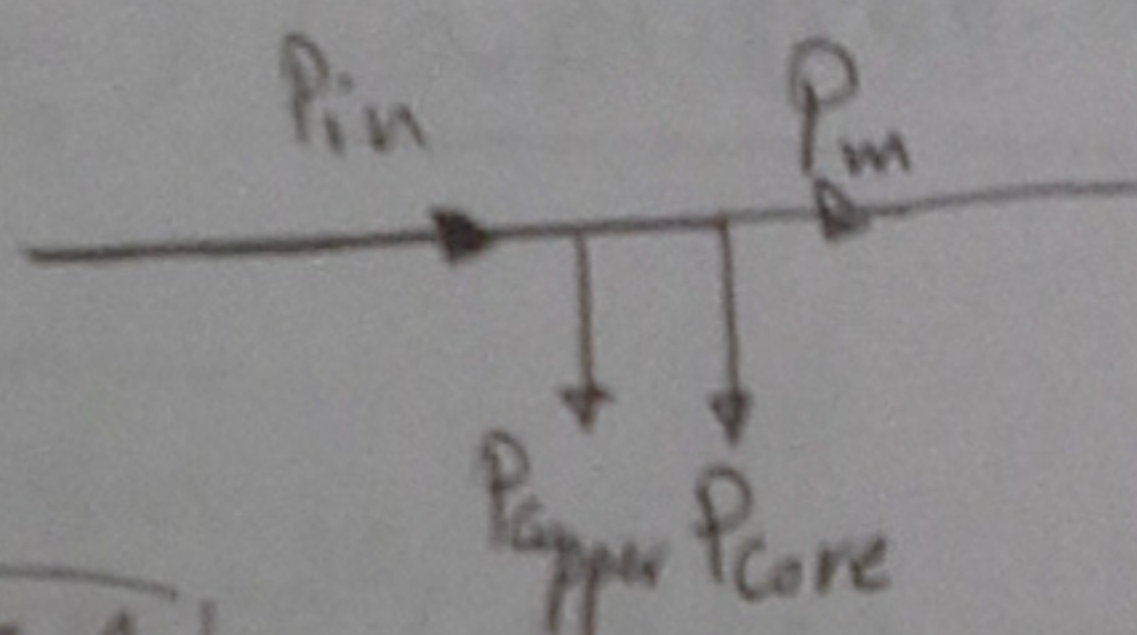

③ $\phi_m = ?$

$\therefore E_1 = 4.44 f \phi_m N_1$

$400 = 4.44 \times 50 \times \phi_m \times 500$

$\therefore \phi_m = \boxed{3.6036 \text{ mwb}}$

for problem ②

$P_{\text{paper}} = I_1^2 R_1 = \left(\frac{15 \times 10^3}{110} \right)^2 \times 0.008875 = \boxed{165.031 \text{ watt}}$

لا بد ان يكونوا متساويين

or

$P_{\text{paper total}} = I_1^2 R_1 + I_2^2 R_2$

$= \left(\frac{15000}{2200} \right)^2 \times 1.75 + \left(\frac{15000}{110} \right)^2 \times 0.0045 = \boxed{165.031 \text{ W}}$

problem 2) 15KVA, 2200/110V, has $R_1 = 1.75 \Omega$, $R_2 = 0.0045 \Omega$
 $X_1 = 2.6 \Omega$, $X_2 = 0.0075 \Omega$

الكل

الى زاوية اليه

a) R_t Referred to primary

$$R_1 = 1.75 \Omega, R_2' = 0.0045 \times \left(\frac{2200}{110} \right)^2 = 1.8 \Omega$$

$$\therefore R_{t|_{pri}} = R_1 + R_2' = \boxed{3.55 \Omega}$$

الى طالع فيه

b) R_t Referred to secondary

$$R_2 = 0.0045 \Omega, R_1' = 1.75 \times \left(\frac{110}{2200} \right)^2 = 4.375 \times 10^{-3} \Omega$$

$$\therefore R_{t|_{sec}} = 8.875 \times 10^{-3} = \boxed{0.008875 \Omega}$$

c) X_t Referred to primary

$$X_1 = 2.6 \Omega, X_2' = 0.0075 \times \left(\frac{2200}{110} \right)^2 = 3 \Omega$$

$$\therefore X_{t|_{prim}} = \boxed{5.6 \Omega}$$

d) X_t Referred to secondary

$$X_2 = 0.0075 \Omega, X_1' = 2.6 \times \left(\frac{110}{2200} \right)^2 = 6.5 \times 10^{-3} \Omega$$

$$\therefore X_{t|_{sec}} = \boxed{0.014 \Omega}$$

e) Z_t Ref. to primary

$$Z_{t|_{prim}} = \sqrt{(R_{t|_{prim}})^2 + (X_{t|_{prim}})^2} = \boxed{6.6304 \Omega}$$

f) Z_t Ref. to secondary

$$Z_{t|_{sec}} = \sqrt{(R_{t|_{sec}})^2 + (X_{t|_{sec}})^2} = \boxed{0.01657 \Omega}$$

g) total copper loss

$$P_{copper} = I_1^2 \times R_{t|_{prim}} = \left(\frac{15 \times 10^3}{2200} \right)^2 \times 3.55 = \boxed{165.031 \text{ watt}}$$

check I_{prime} الى زاوية اليه

2

③ 250/125 V XFMR, $S = 5 \text{ kVA}$, 1- ϕ , $R_1 = 0.2 \Omega$, $X_1 = 0.75 \Omega$
 $R_2 = 0.05 \Omega$, $X_2 = 0.2 \Omega$

① Regulation for full load on 0.8 P.f lead

② V_2 on full load and 0.8 P.f lead

$R_1 = 0.2 \Omega$, $X_1 = 0.75 \Omega$, $R_2 = 0.05 \Omega$, $X_2 = 0.2 \Omega$, $\cos \phi = 0.8$ leading

① → Referred to secondary.

$$R_1' = R_1 \times \left(\frac{125}{250} \right)^2 = 0.05 \Omega$$

$$\therefore R_{tsec} = 0.05 + 0.05 = 0.1 \Omega$$

$$X_1' = X_1 \times \left(\frac{125}{250} \right)^2 = 0.1875 \Omega$$

$$\therefore X_{t|sec} = 0.3875 \Omega$$

$$I_{sec} = \frac{S}{V_{sec}} = \frac{5 \times 10^3}{125} = 40 \text{ A} = I_2$$

$$\%R = \frac{I_2 R_{tsec} \cos \phi \pm I_2 X_{tsec} \sin \phi}{V_2} \times 100$$

→ Lag P.f
→ Lead P.f

$$\phi = \cos^{-1}(0.8) = 36.869^\circ$$

$$\therefore \sin \phi = 0.6$$

$$\therefore \%R = \frac{40 \times 0.1 \times 0.8 - 40 \times 0.3875 \times 0.6}{125} \times 100$$


② The same load

$$\%R = \frac{V_2 - V_{2t}}{V_2} \Rightarrow -4.88 = \frac{125 - V_{2t}}{125}$$

→ Terminal Voltage

$$\therefore V_{2t} = 131.1 \text{ V}$$

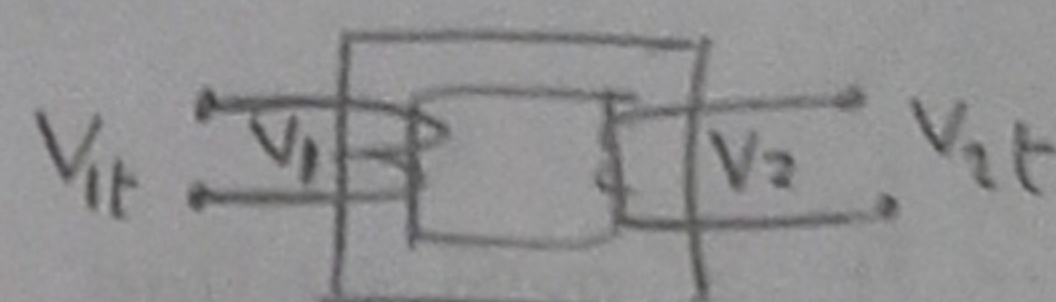Leading P.f $\therefore V_{2t} < V_2$ i.e. 131.1 V
 (2 lines)



Lead \sim L.C

$$\times 100 = -4.88\%$$

problem 4) $S = 4 \text{ KVA}$, $200/400 \text{ V}$, 50 Hz XFMR, $1-\phi$

$$R_{t\text{prim}} = 0.15 \Omega, \text{ iron loss} = 60 \text{ W}$$

① $P_{\text{copper total}}$ on full load

② η full-load at 0.9 P.f lag

③ η half-load at 0.8 P.f lead

المحل

$$V_1 = 200 \text{ V}, V_2 = 400 \text{ V}, R_{t\text{pr}} = 0.15, P_i \Rightarrow 0 \text{ or } P_{\text{core}} = 60 \text{ W}$$

①

$$\therefore R_{t\text{sec}} = 0.15 \times \left(\frac{400}{200}\right)^2 = 0.6 \Omega \text{ Referred to secondary}$$

$$I_{2\text{fL}} = \frac{S}{V_2} = \frac{4000}{400} = 10 \text{ A}$$

$$\therefore P_{\text{copper}} = I_{2\text{fL}}^2 \times R_{t\text{sec}} = 10^2 \times 0.6 = 60 \text{ W} \quad \# \text{ or } \left(\frac{2000}{200}\right)^2 \times 0.15 = 60 \text{ W}$$

$$\textcircled{2} \therefore \eta = \frac{S \cos \phi}{S \cos \phi + P_i + P_{\text{copper(fL)}}}$$

$\therefore \eta$ at $\cos \phi = 0.9 \text{ Lag (full-load)}$

$$\therefore \eta = \frac{4 \times 10^3 \times 0.9}{4 \times 10^3 \times 0.9 + 60 + 60} \times 100 = 96.77\%$$

③ when the load reduced to half

$n = \frac{\text{actual load}}{\text{full load}} = \text{fraction by which load is less than full-load}$

وعندما ينزاد التحميل ينقص التيار بنفس النسبة
وبالتالي ينقص P_{copper} وايضاً $P_{\text{out}} \propto V_2 I_2 \cos \phi \propto P_{\text{out}} \propto I_2^2 \propto n^2 P_{\text{copper(fL)}}$, $P_{\text{out new}} = n P_{\text{out(fL)}}$

$$\therefore \eta = \frac{n \times S \times \cos \phi}{n \times S \times \cos \phi + P_i + n^2 P_{\text{copper(fL)}}} = \frac{0.5 \times 4 \times 10^3 \times 0.8}{0.5 \times 4 \times 10^3 \times 0.8 + 60 + (0.5^2) \times 60}$$

$$\therefore \eta = 95.52\%$$

~~2000/200~~

④

problem 5) 5 KVA , $500/250$
O.C. Test: 500 V ,
S.C. Test: 25 V , 10
① Full-load, 0.8 lag P.f ② $\% R_{\text{sc}}$
④ Draw Eqn. out ref. to primary winding
primary winding $V_{\text{sc}} = 25 \text{ V}$ $I_{\text{sc}} = 10 \text{ A}$
→ from O.C. Test $V_{\text{nl}} = 500 \text{ V}$
 $I_c = I_{\text{nl}} \cos \phi_{\text{nl}}$
 $I_m = I_{\text{nl}} \sin \phi_{\text{nl}}$

Problem 5) 5 KVA, 500/250 V, 1- ϕ 50 Hz

O.C. Test: 500V, 1A, 50W (L.V. side open)

S.C. Test: 25V, 10A, 60W (L.V. side shorted)

- ① η Full-load, 0.8 lag P.F. ② $\%R_{f.L}$, 0.8 P.F. lead ③ η at 60% of f.l., 0.8 lead P.F.
 ④ Draw Eqn. ext. ref. to primary with full data.

primaries, $V_{n.L}$ $I_{n.L}$ $P_{n.L}$ $V_{s.c}$ $I_{s.c}$ $P_{s.c}$ $V_{n.L}$ $I_{n.L}$ $P_{n.L}$ $V_{s.c}$ $I_{s.c}$ $P_{s.c}$

→ From O.C. Test $V_{n.L} = 500V$, $I_{n.L} = 1A$, $P_{n.L} = 50W$

$$I_c = I_{n.L} \cos \phi_{n.L}$$

$$I_m = I_{n.L} \sin \phi_{n.L}$$

where

$$\cos \phi_{n.L} = \frac{P_{n.L}}{V_{n.L} I_{n.L}} = \frac{50}{500 \times 1} = 0.1$$

$$\therefore I_c = 0.1A$$

$$\phi_{n.L} = \cos^{-1}(0.1) = 84.26^\circ$$

$$\therefore \sin \phi_{n.L} = 0.99498$$

$$\therefore I_m = 0.99498A$$

$$\therefore X_m = \frac{V_{n.L}}{I_m} = \frac{500}{0.99498} = 502.52 \Omega$$

at O.C. Test $P_{n.L} = P_{core} = P_{iron loss} = 50W$

→ from S.C. test

$V_{s.c} = 25V$, $I_{s.c} = 10A$, $P_{s.c} = 60W$

$$\therefore P_{s.c} = I_{s.c}^2 \times R_{eq.pri} = P_{copper (f.l.)}$$



$$\therefore R_{eq.pri} = \frac{P_{s.c}}{I_{s.c}^2} = \frac{60}{(10)^2} = 0.6 \Omega$$

from Loop ①

$$V_{s.c} = I_{s.c} (R_{eq.pri} + j X_{eq.pri}) = Z_{eq} \times I_{s.c}$$

$$\therefore Z_{eq} = \frac{V_{s.c}}{I_{s.c}} = \frac{25}{10} = 2.5 \Omega$$
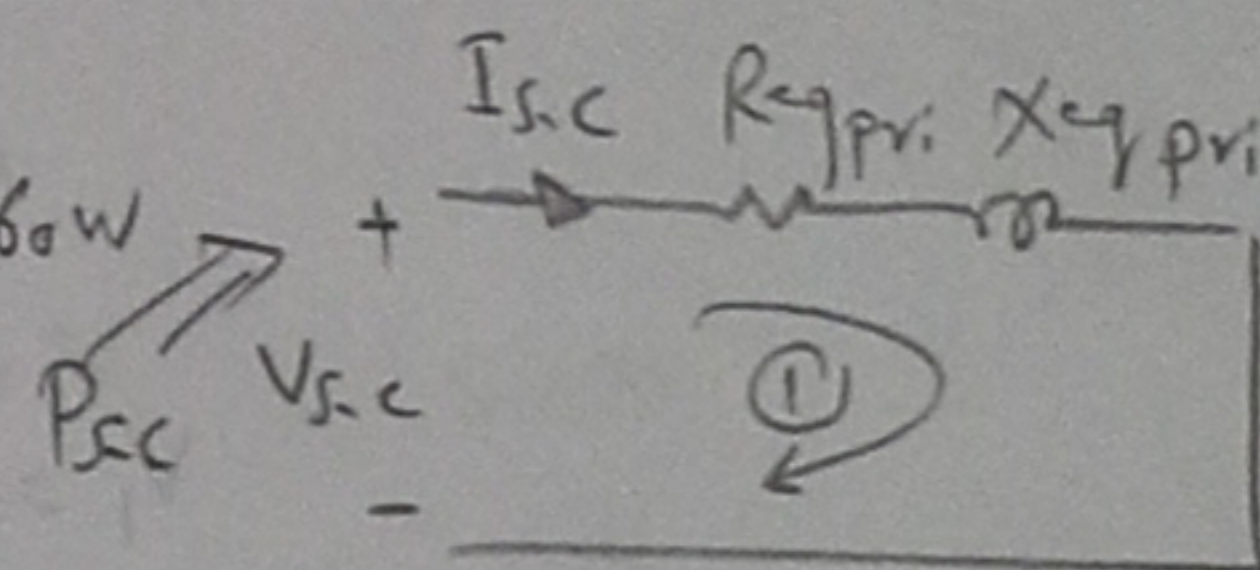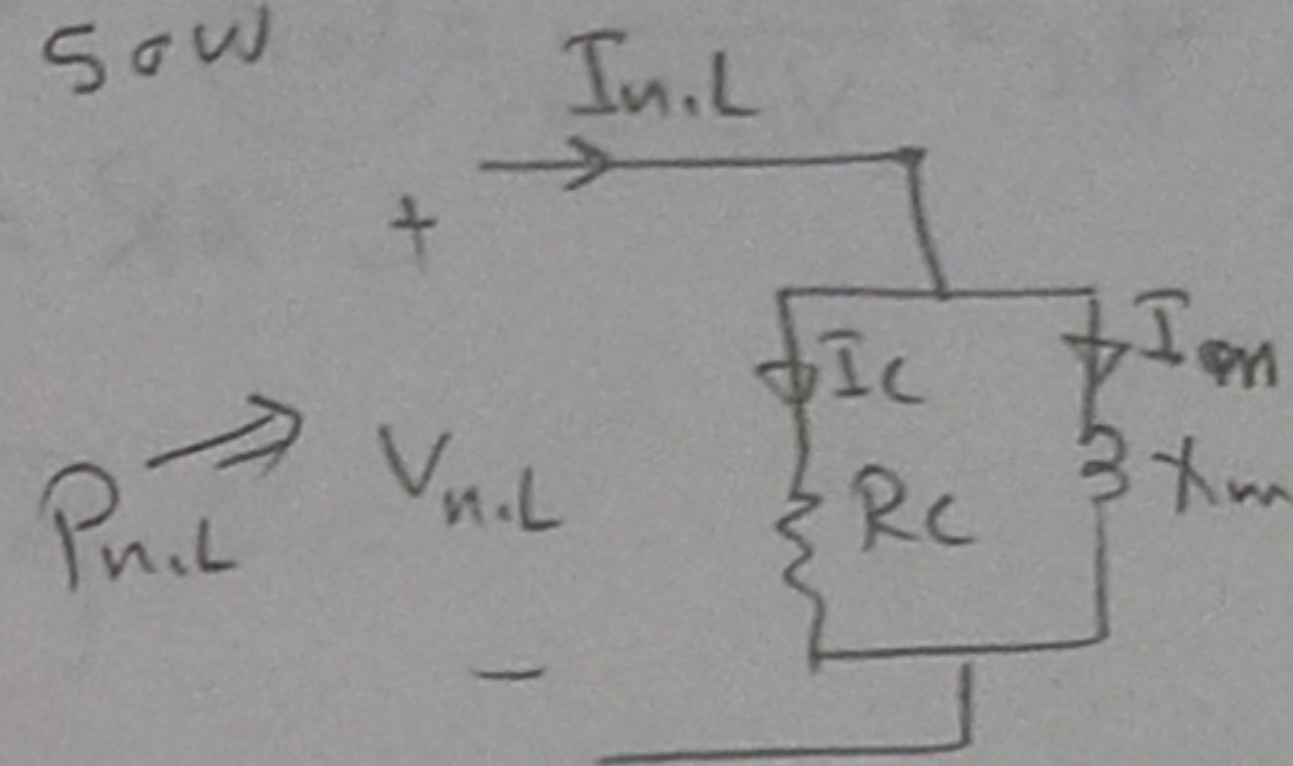
$$X_{eq.pri} = \sqrt{Z_{eq}^2 - R_{eq}^2} = 2.4269 \Omega$$



أقدرا قولنا $I_{f.L} = I_{s.c}$
 لأن $I_{f.L} = I_{s.c}$
 $I_{f.L} = \frac{5 \times 10^3}{500} = 10A$

$$\textcircled{1} \eta_{f.L, 10.8 \text{ pf}} \quad \therefore \eta = \frac{S \times \cos \phi_{f.L}}{S \times \cos \phi_{f.L} + P_i + P_{cu f.L}} \times 100$$

$$\therefore \eta = \frac{5 \times 10^3 \times 0.8}{5 \times 10^3 \times 0.8 + 50 + 60} \times 100 = \boxed{97.32\%}$$

$$\textcircled{2} \%R_{f.L, 10.8 \text{ pf}} \quad \therefore \%R = \frac{I_{f.L} R_{tpri} \cos \phi - I_{f.L} X_{tpri} \sin \phi}{V_1} \times 100$$

$$I_{f.L} = \frac{S \times 10^3}{V_1 = 500} = 10 \text{ A}$$

$$\therefore \%R = \frac{10 \times 0.6 \times 0.8 - 10 \times 2.4269 \times 0.6}{500} \times 100$$


$$\therefore \%R = \boxed{-1.95\%}$$

$$\textcircled{3} \eta_{60\% f.L, 10.8 \text{ pf lead}} \quad n = \frac{60\%}{100\%} = 0.6$$

$$\therefore \eta = \frac{0.6 \times 5 \times 10^3 \times 0.8}{0.6 \times 5 \times 10^3 \times 0.8 + 50 + (0.6)^2 \times 60} \times 100$$

$$\therefore \eta = \boxed{97.103\%}$$

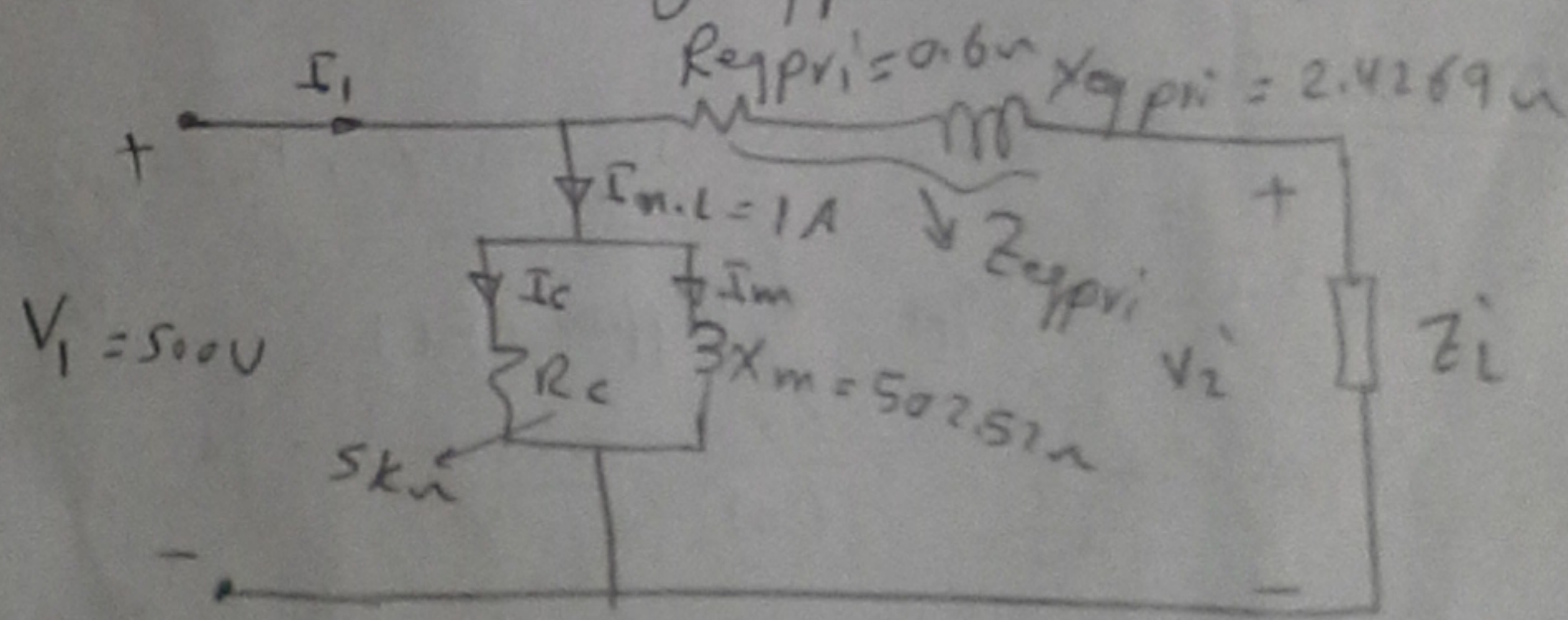④ Eqn. CKT Referred to primary using approximately Eqn. CKT



problem ⑥ like ⑤ but $P_{cu \text{ pf.L}}$ should be Calculated

Ex (7) (17) 2500/250 V, 1- ϕ , 50 Hz, 50 KVA = S

$$R_1 = 0.8 \Omega, R_2 = 0.012 \Omega, X_1 = 4 \Omega, X_2 = 0.04 \Omega$$

$$\eta_{\max} = 96\% \text{ at } 75\% \text{ f.l at } P.f = 1 = \cos \phi$$

$$I_m = 1.2 \text{ A on } 2500 \text{ V side}$$

Req: O.C. Test, S.C. Test Readings if supply is given to 2500 V side



→ Refer parameters to H.V side (primary)

$$R_{eq} = R_1 + R_2' = 0.8 + 0.012 \left(\frac{2500}{250} \right)^2 = 2 \Omega$$

$$X_{eq} = X_1 + X_2' = 4 + 0.04 \left(\frac{2500}{250} \right)^2 = 8 \Omega$$

→ for max. η $P_{\text{iron core}} = P_{\text{copper}} \therefore P_i = P_{cu}$

$$\eta_{\max} = \frac{n \times S \times \cos \phi}{n \times S \times \cos \phi + 2 P_i} \times 100, n = \frac{75\%}{100\%} = 0.75$$

$$\therefore 0.96 = \frac{0.75 \times 50 \times 10^3 \times 1}{0.75 \times 50 \times 10^3 \times 1 + 2 P_i}$$

$$\therefore P_i = 781.25 \text{ W} \rightarrow P_{\text{iron core loss}}$$

→ for O.C Test, $V_{n.L}, I_{n.L}, P_{n.L}$

the applied voltage is rated $\therefore V_{n.L} = V_1 = 2500 \text{ V}$

$$P_{n.L} = P_{\text{iron}} = 781.25 \text{ W}$$

$$\textcircled{1} \leftarrow I_m = 1.25 = I_{n.L} \sin \phi_{n.L} \quad P_{n.L} = V_{n.L} I_{n.L} \cos \phi_{n.L}$$

$$\textcircled{2} \leftarrow I_{n.L} \cos \phi_{n.L} = 0.3125 \quad \therefore \cos \phi_{n.L} I_{n.L} = \frac{P_{n.L}}{V_{n.L}}$$

$$\frac{1.25}{0.3125} = \frac{I_{n.L} \sin \phi_{n.L}}{I_{n.L} \cos \phi_{n.L}} \quad \text{مقابلته}$$

$$\therefore \tan \phi_{n.L} = 3.84 \quad \therefore \phi_{n.L} = 75.4^\circ$$

$$\therefore I_{n.L} = \frac{0.3125}{\cos(75.4)} = 1.239 \text{ A}$$

∴ the open circuit readings are

$$V_{n.L} = 2500V, I_{n.L} = 1.239A, P_{n.L} = 781.25W$$

→ for the s.c Test

$$V_{s.c}, I_{s.c}, P_{s.c}$$

$$I_{f.L} = I_{s.c} = \frac{S}{V_1} = \frac{50 \times 10^3}{2500} = 20A$$

$$P_{s.c} = I_{f.L}^2 \times R_{eq} = 20^2 \times 2 = 800W$$

$$Z_{eq} = \sqrt{R_{eq}^2 + X_{eq}^2} = \sqrt{2^2 + 8^2} = 8.2462 \Omega$$


$$\therefore Z_{eq} = \frac{V_{s.c}}{I_{s.c}} \quad \therefore V_{s.c} = Z_{eq} \times I_{s.c}$$

$$\therefore V_{s.c} = 164.924V$$

∴ The Short Circuit readings are

$$V_{s.c} = 164.924V, I_{s.c} = 20A, P_{s.c} = 800W \quad \#$$

① أرد مسأله من الكتاب 220 440

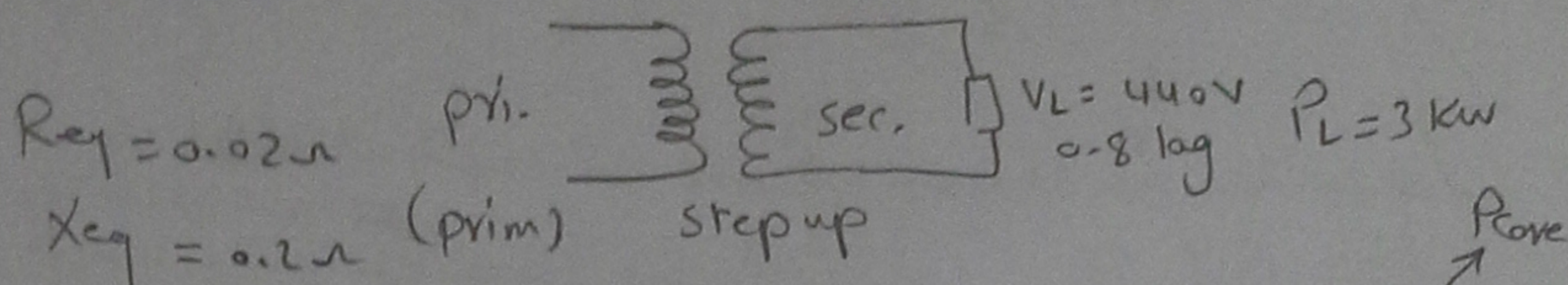

O.C. at primary $V_{n.L} = 220V$, $I_{n.L} = 1.8A$, $P_{n.L} = 39.6W$

Req, η , γ, R

$$V_L' = V_L \left(\frac{220}{440} \right) = 220V$$

$$V_L' = 220 \angle 0^\circ V$$

$$I_2' = \frac{P_L}{V_L' \text{ P.f.}} = \frac{3000}{220 \times 0.8}$$

$$\therefore I_2' = 17.045 \angle -36.87^\circ A$$

$$V_1 = E = I_2' (R_{eq} + jX_{eq}) + V_L' = 17.045 (0.02 + j0.2) + 220 \angle 0^\circ$$

$$V_1 = E = 222.3324 \angle 0.65^\circ V$$

$$I_1 = I_{n.L} + I_2'$$

$$\downarrow$$

$$E$$

$$Z_{n.L} \rightarrow \left(\frac{R_c + jX_m}{R_c + X_m} \right)$$

$$I_c = I_{n.L} \cos \phi_{n.L} = 0.18$$

$$I_m = I_{n.L} \sin \phi_{n.L} = 1.791$$

$$\cos \phi_{n.L} = \frac{P_{n.L}}{V_{n.L} I_{n.L}} = 0.1$$



$$\therefore \phi_{n.L} = 84.26^\circ$$

$$\therefore \sin \phi_{n.L} = 0.9949$$

$$R_c = \frac{V_{n.L}}{I_c} = 1222.22 \Omega$$

$$X_m = \frac{V_{n.L}}{I_m} = 122.836 \Omega$$
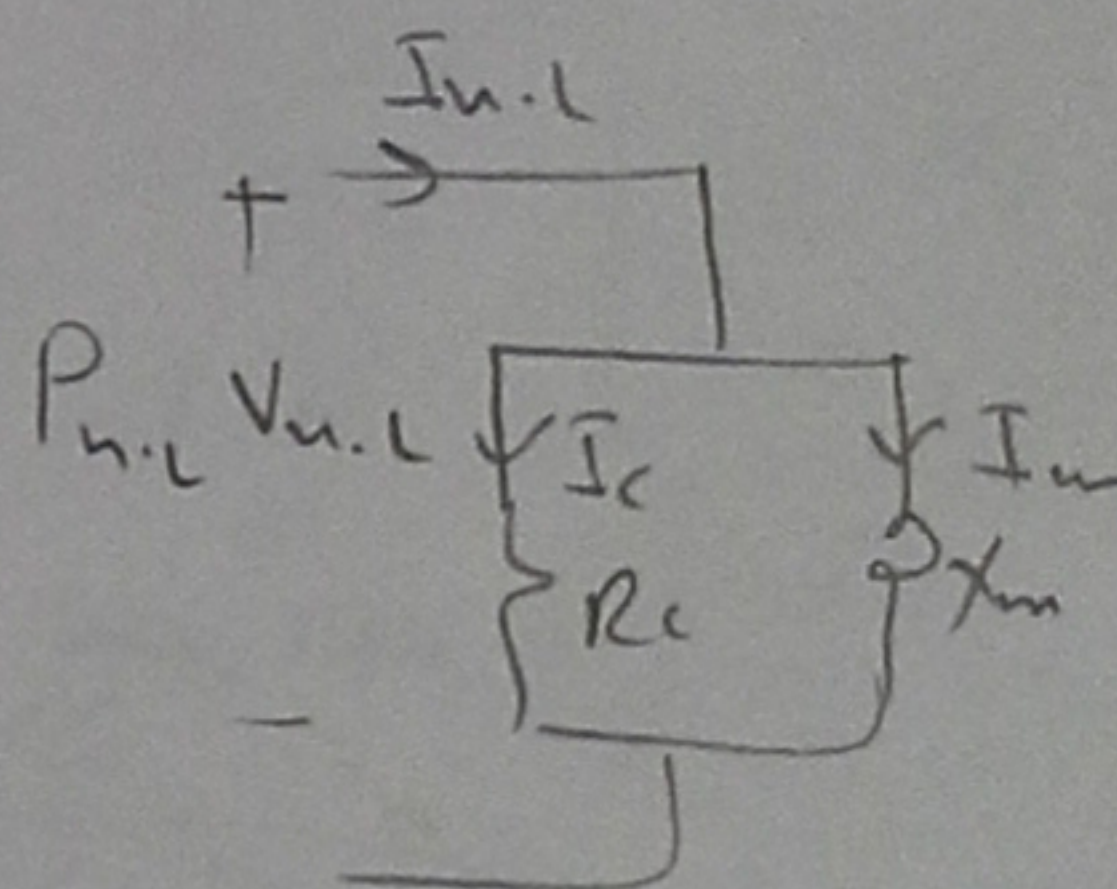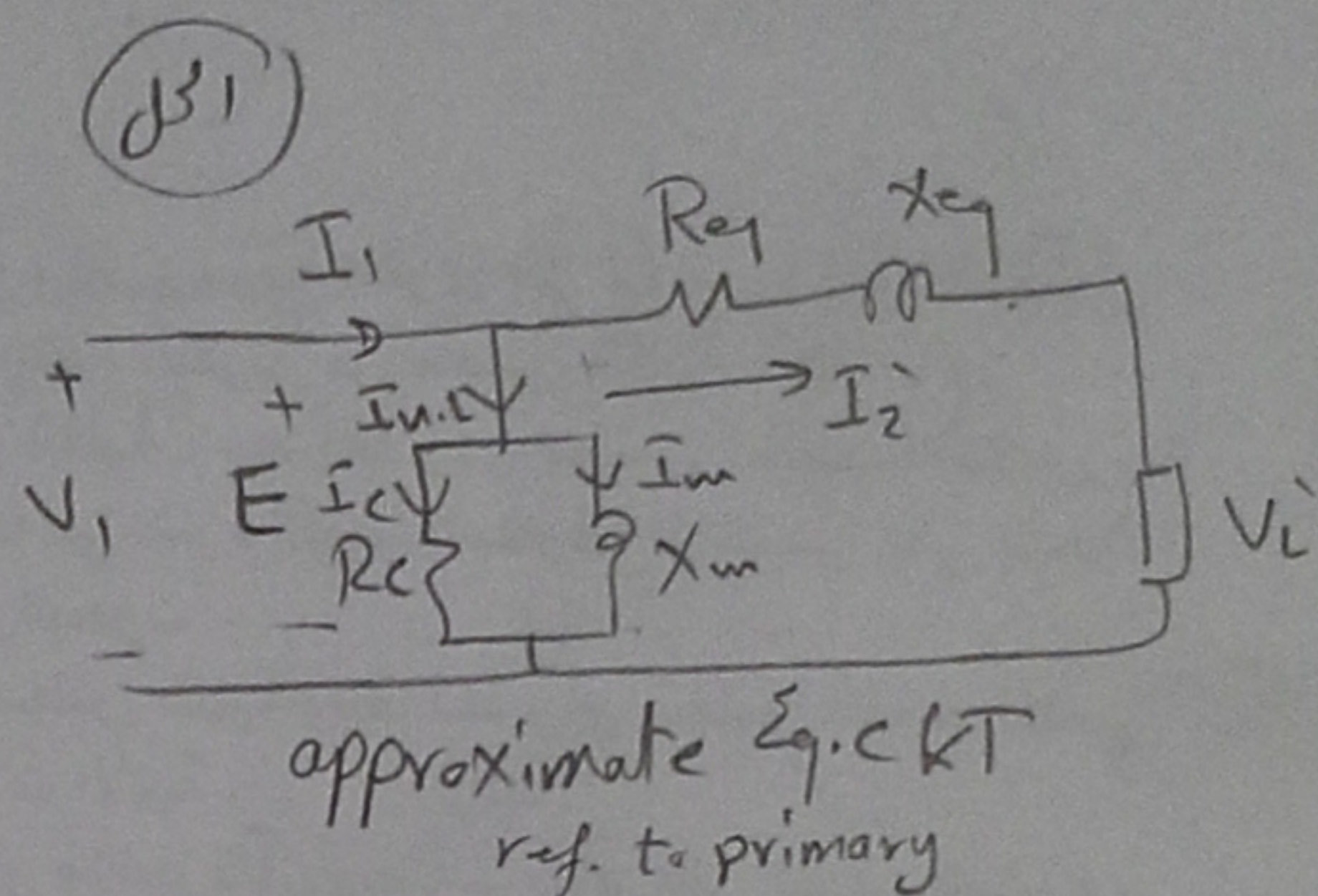
$$Z_{branch} = 122.22 \angle 84.261^\circ = \frac{R_c jX_m}{R_c + jX_m}$$



$$\bar{I}_{n.L} * Z_{branch} = E$$

$$\therefore \bar{I}_{n.L} = 1.8 \angle -83.611^\circ \text{ A}$$

$$\therefore \bar{I}_1 = \bar{I}_{n.L} + \bar{I}_2' = 18.34 \angle -41^\circ \text{ A}$$

$$\therefore P_{in} = V_1 \bar{I}_1 \cos(\theta_v - \theta_i) = 3046.84 \text{ W}$$

$$P_{out} = \bar{I}_2' V_L \cos(\theta_v - \theta_i) = P_L = 3000 \text{ W}$$

$$\boxed{\eta = 98.45\%}$$

$$\%V_R = \frac{V_{n.L} - V_{R.L}}{V_{R.L}} \times 100 = \frac{222.3324 - 220}{220}$$

$$\boxed{\%V_R = 1.06\%}$$